

SystemC RTL Multiplier and Approximate Multiplier Report

University of Tehran – Electrical and Computer Engineering Department

Course: Object-Oriented Modeling of Electronic Circuits (ECE 342 - Spring 1404)

Students : Amir Abbas Moumeni Zadeh – Mahdis Mirzaei

Due Date: Ordibehesht 19, 1404

1. Objective

The goal of this project is to develop a Radix-2 sequential 8-bit multiplier and incorporate it into a 16-bit approximate multiplier (VAM16). The final design includes both RTL-level and BFM-level models, implemented and tested using SystemC.

2. Part 1 – 8-bit Sequential Multiplier

2.1 Design Description

This module multiplies two 8-bit inputs, **A** and **B**, producing a 16-bit output **W**. It uses **startB** and **readyB** handshaking and runs on a positive clock edge with asynchronous reset.

2.2 Interface


- **Inputs:**
A[7:0], B[7:0], clk, rst, startB
- **Outputs:**
W[15:0], readyB

2.3 SystemC Code Overview

```
SC_MODULE(Multiplier) {  
    sc_in<bool> clk, rst, startB;  
    sc_in<sc_uint<8>> A, B;  
    sc_out<sc_uint<16>> W;  
    sc_out<bool> readyB;  
    // ...  
};
```

Behavior:

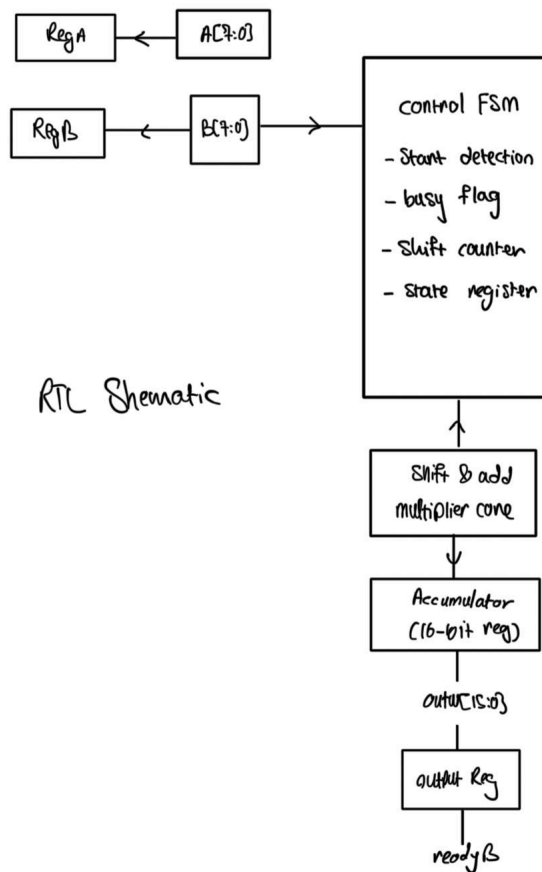The `multiply_process()` method is triggered on clock edges. When `startB` is high, the multiplier loads inputs, performs multiplication, and asserts `readyB` when done.



3. Part 2 – Approximate Multiplier (VAM16)

3.1 Concept

The VAM16 design extracts the most significant 8-bit portion of each 16-bit operand, based on the position of the first '1' from the left. It multiplies the 8-bit segments using the base multiplier and left-shifts the result according to the number of ignored bits, producing a 16-bit approximate output.

3.2 SystemC Module Structure

cpp

CopyEdit


```
SC_MODULE(ApproxMultiplier) {
    sc_in<sc_uint<16>> A, B;
```

```

sc_out<sc_uint<16>> W;
sc_in<bool> start, clk, rst;
sc_out<bool> ready;
// Internal signals and 8-bit multiplier instance
};

```

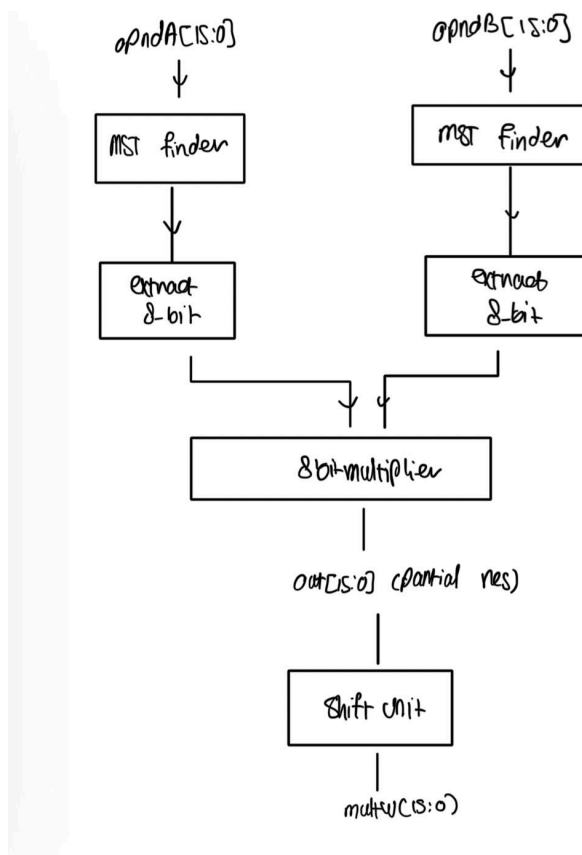- Extracts 8-bit segments using bitwise scan
- Feeds segments into **Multiplier**
- Shifts result left by ignored bits



4. Part 3 – Bus Functional Model (BFM)

4.1 BFM Description

ApproxMulBFM models the approximate multiplier's behavior cycle-accurately using SystemC's CTHREAD mechanism. It reads `start_sig`, performs the MSB extraction, multiplication, and zero-padding, and drives `ready_sig` and `out_mul`.

4.2 Code Overview

```
SC_MODULE(ApproxMulBFM) {  
    sc_in_clk clk;  
    sc_in<bool> reset_n;  
    sc_in<sc_logic> start_sig;  
    sc_out<sc_logic> ready_sig;  
    sc_in<sc_lv<16>> in_A, in_B;  
    sc_out<sc_lv<16>> out_mul;  
  
    void run(); // Main process  
};
```

4.3 Helper Function

```
unsigned int count_leading_zeros(unsigned int value) const;
```

This function aids in determining the bit range to extract from each operand.

5. Simulation and Testing

5.1 Testbench Summary

Each module was tested using a dedicated testbench to validate:

- Correctness of output
 - Proper handshaking
 - Cycle-accurate response in BFM
-

6. Conclusion

This project implemented a SystemC-based RTL multiplier and extended it into an approximate 16-bit multiplier with hardware-efficient design. The BFM model successfully mimics the hardware behavior for simulation and testing purposes. The project demonstrates effective modular design and verification methodology in SystemC.
